

# Chapter 3: Current and Resistance. Direct Current Circuits

3.1. Electric Current

3.2. Resistance and Resistivity

3.3. Ohm's Law and a Microscopic View of Ohm's Law

3.4. Semiconductors and Superconductors

3.5. Work, Energy, and Emf

3.6. Kirchhoff's Rules

3.7. Resistors in Series and in Parallel

3.8. RC Circuits

## 3.5. Work, Energy, and Emf

### 3.5.1. Concepts:

- To make charge carriers flow through a device we must establish a potential difference between the ends of the device, e.g., connecting the device to a charged capacitor but the duration time is very short
- To produce a steady flow, we need a *charge pump*, an **emf** device  $\mathcal{E}$  (emf: electromotive force, outdated phrase)
- Some examples for emf devices: battery, electric generators (solar cells, fuel cells, thermopiles), living systems (electric eels)





- When an emf is connected (in a closed circuit), **within** the emf device, positive charge carriers move from a region of low electric potential (low electric potential energy, negative terminal) to a region of higher potential (higher potential energy, positive terminal)


- This flow of positive charge and the current have the same direction

- As this motion is the opposite of what the electric field between the terminals would cause the positive charges to move, therefore there must be a energy source to do work on the charges

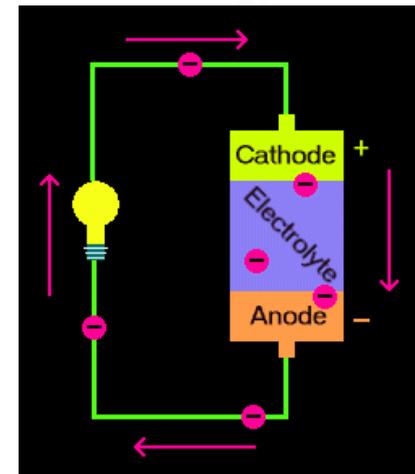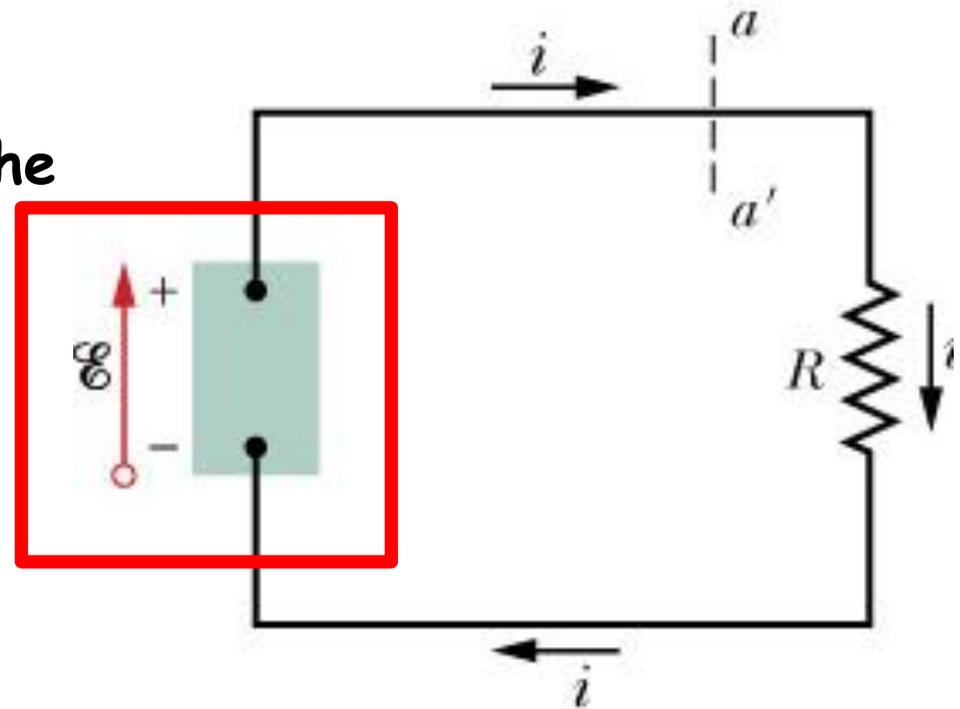- The source may be chemical, or involves mechanical forces, temperature differences, or the Sun



# Hydrogen - Oxygen Fuel Cell

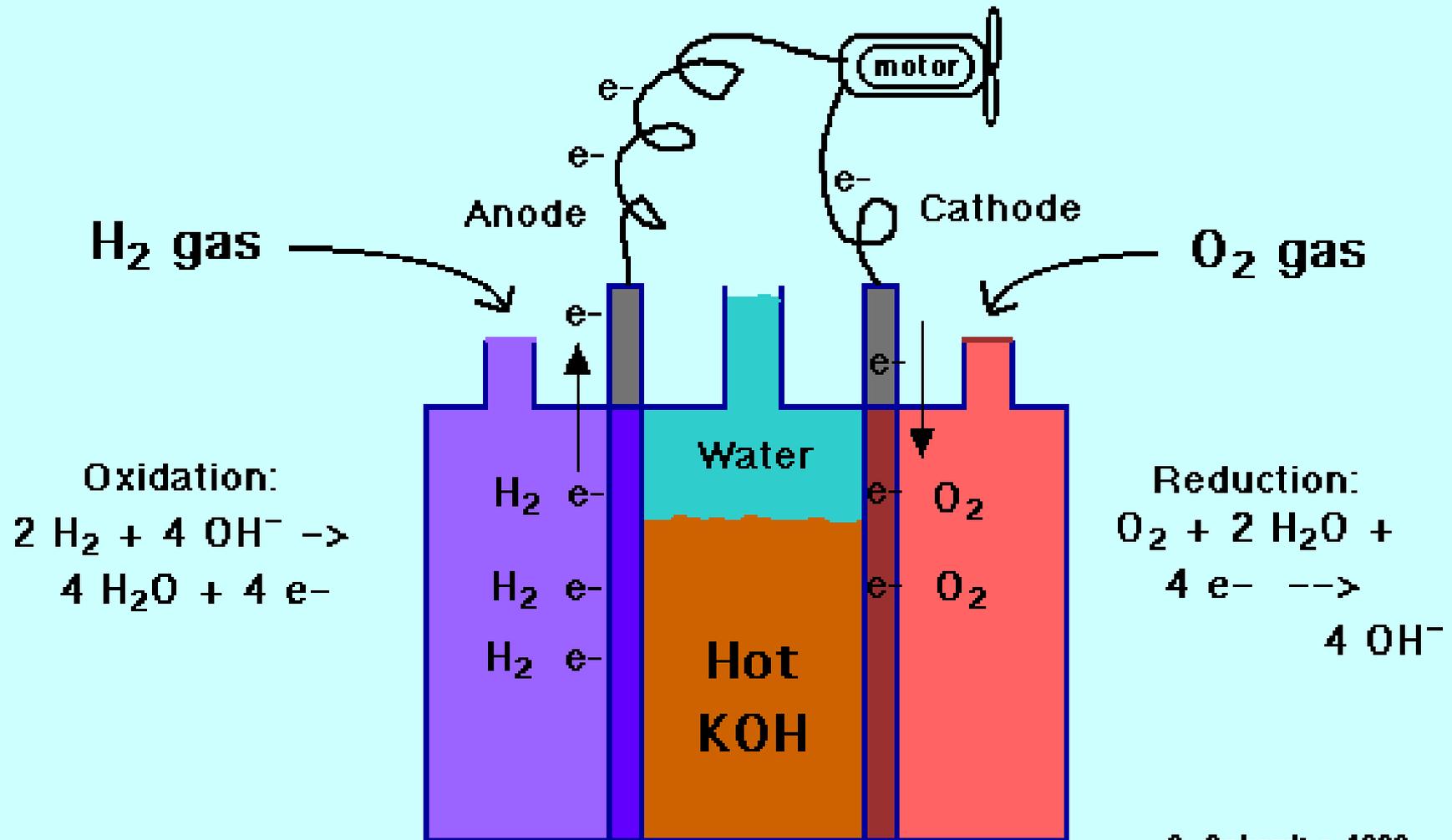



### 3.5.2. Work, Energy, and Emf:

#### Emf $\mathcal{E}$ :

- We analyze a circuit as shown: in any time interval  $dt$ , a charge  $dq$  passes through any cross section of the circuit
- The emf device does an amount of work  $dW$ : we define the emf of the emf device as follows:

$$\mathcal{E} = \frac{dW}{dq}$$

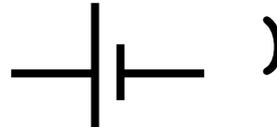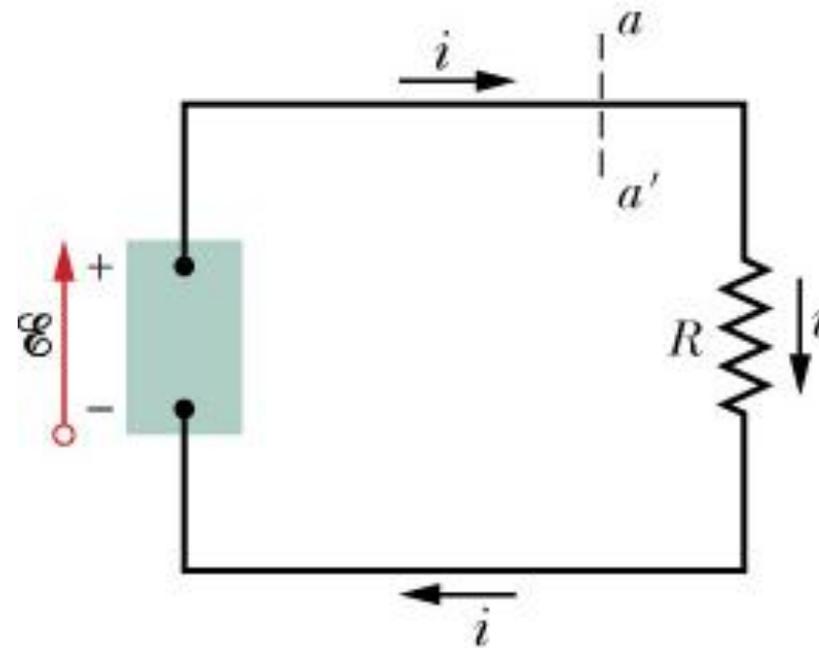- So, the emf of an emf device is the work per unit charge that the device does in moving charge from its low-potential terminal to its high-potential terminal (symbol: )
- **SI unit: 1 Volt (V) = 1 Joule / 1 Coulomb**




- **An ideal emf device:** the potential difference between the terminals is equal to the emf of the device (no internal resistance  $r = 0$ ),  $V = \varepsilon$  (open or closed circuit)
- **A real emf device:**  $V = \varepsilon$  if there is no current through the device and  $V < \varepsilon$  if there is a current, it means the real devices have internal resistance ( $r \neq 0$ )

**Power of an emf device:**

$$dW = \varepsilon dq = \varepsilon i dt = P dt$$

$$P = i \varepsilon$$

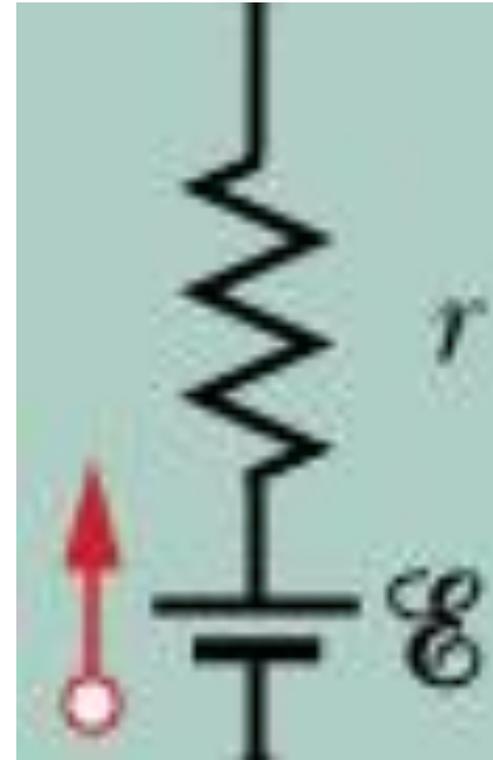


A real emf device

## 3.6. Kirchhoff's Rules

**3.6.1. Loop Rule (Voltage Law):** The algebraic sum of the changes in potential encountered in a complete traversal of any loop of a circuit must be zero

**Example:** We consider a circuit as shown, from point **a** we follow the clockwise direction, we have:

$$\mathcal{E} - iR = 0$$

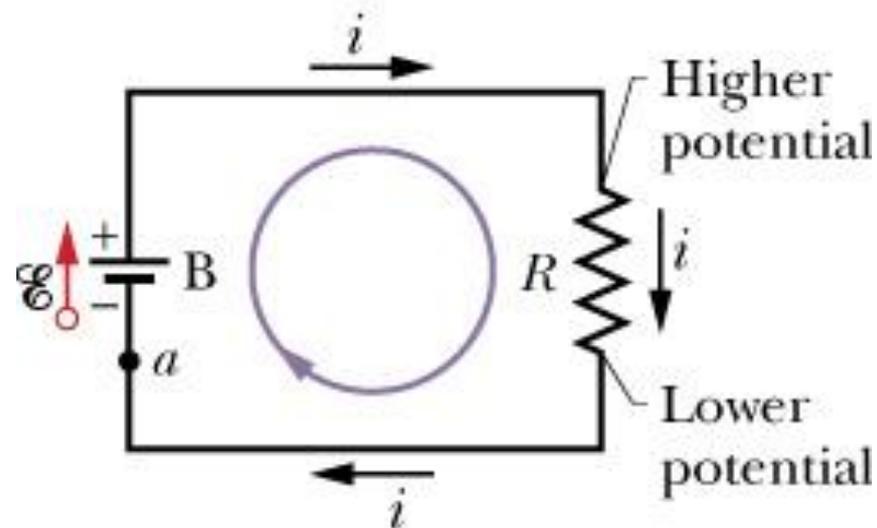


### Important Notes:

- For a move through a resistance in the direction of the current, the change in potential is  $-iR$ ; in the opposite direction it is  $+iR$  (resistance rule)
- For a move through an ideal emf device in the direction of the emf arrow, the change in potential is  $+\mathcal{E}$ ; in the opposite direction it is  $-\mathcal{E}$  (emf rule)


- If you follow the counterclockwise direction:

$$iR - \mathcal{E} = 0$$

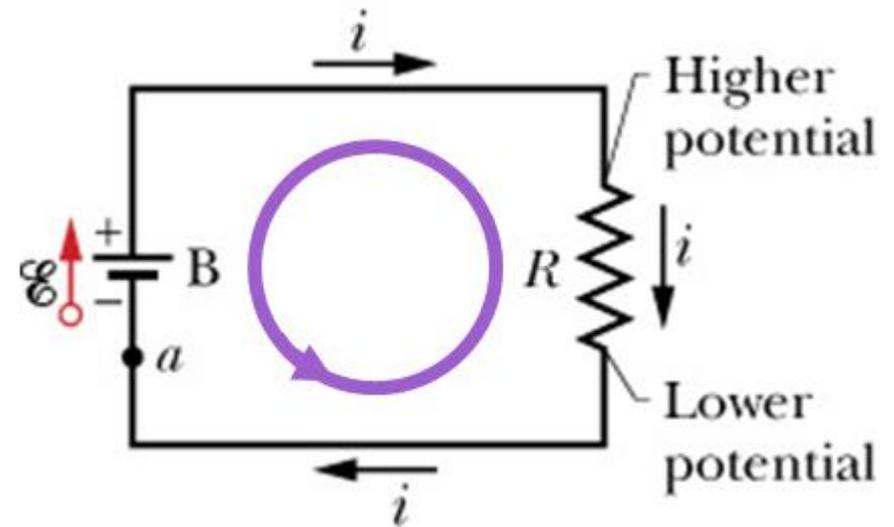

**Checkpoint:** The figure shows the current  $i$  in a single-loop circuit with a battery  $B$  and a resistance  $R$  (and wires of negligible resistance). (a) Should the emf arrow at  $B$  be drawn pointing leftward or rightward? At points  $a$ ,  $b$ , and  $c$ , rank (b) the magnitude of the current, (c) the electric potential, and (d) the electric potential energy of the charge carriers, greatest first.


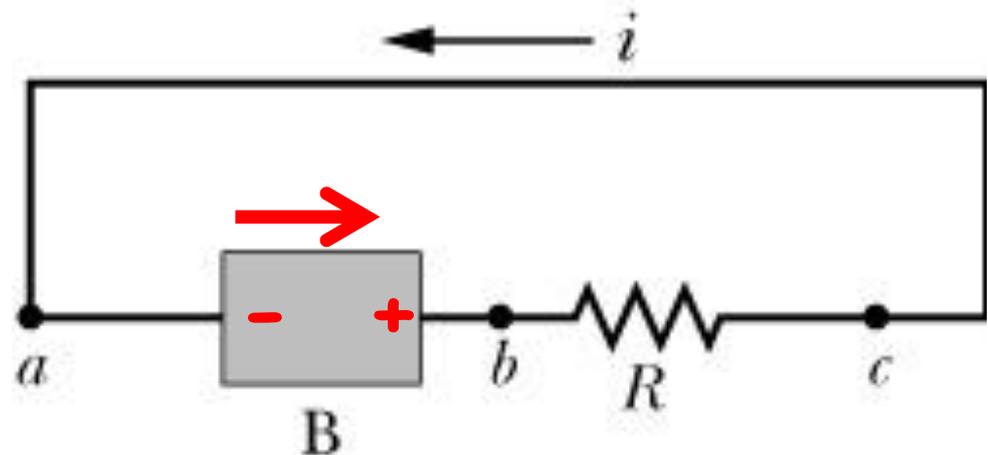
- (a) rightward
- (b) all tie
- (c)  $V_b, V_a = V_c$
- (d)  $b, a = c$



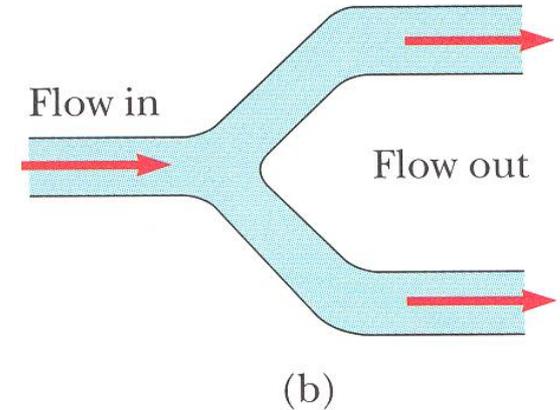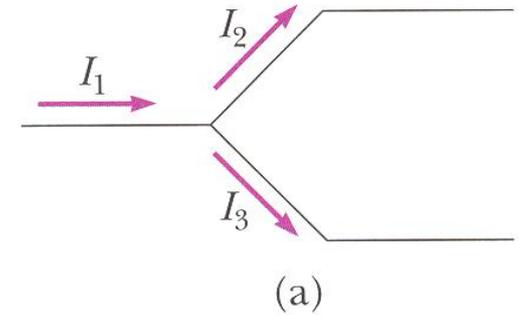**3.6.2. Junction Rule (Current Law):** The sum of the currents entering any junction must be equal to the sum of the currents leaving that junction

$$i_1 = i_2 + i_3$$

This rule is a statement of the conservation of charge for a steady flow of charge, there is neither a buildup nor a depletion of charge at a junction



### 3.7. Resistors in Series and in Parallel:

In this section, we study resistances in series and in parallel using Kirchhoff's rules. First, we apply the rules for a single-loop circuit

#### 3.7.1. A single-loop circuit:

##### Internal Resistance:

➤ A real battery has internal resistance  $r$

Using the loop rule clockwise beginning at point  $a$ :


$$V_b - V_a + V_d - V_c = 0$$

As the battery has a resistance  $r$ :  $V_b - V_a = \mathcal{E} - ir$


$$(\mathcal{E} - ir) + (-iR) = 0$$

So, we can calculate the current  $i$ :

$$i = \frac{\mathcal{E}}{r + R}$$

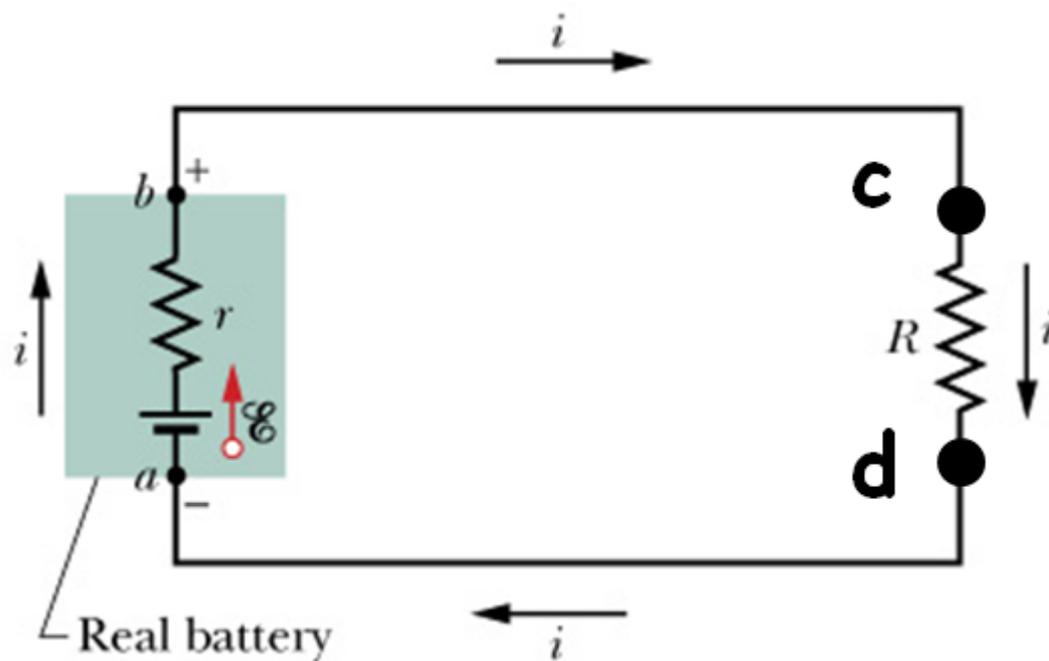
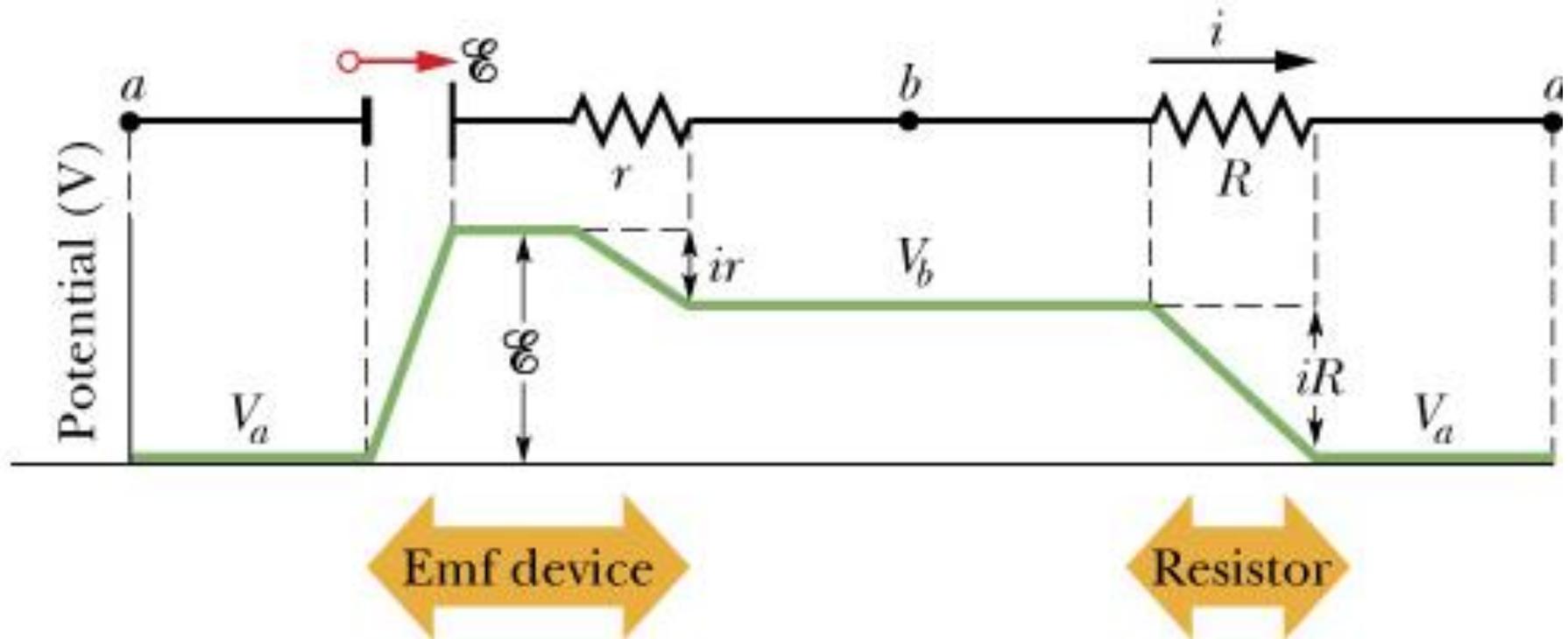
## The changes in electric potential around the circuit



**Note:** in general, if a battery is not described as real or if no internal resistance is indicated, you can assume that it is ideal

### 3.7.2. Multiloop circuits:

**Example:** The figure shows a multiloop circuit consisting of three branches

Junction rule for point b:

$$i_1 + i_3 = i_2 \quad (1)$$


Applying the loop rule for left-hand loop badb in a counter-clockwise direction:

$$\varepsilon_1 - i_1 R_1 + i_3 R_3 = 0 \quad (2)$$

For right-hand loop bdcdb:  $-i_3 R_3 - i_2 R_2 - \varepsilon_2 = 0 \quad (3)$

For big loop badcb:  $\varepsilon_1 - i_1 R_1 - i_2 R_2 - \varepsilon_2 = 0 \quad (4)$

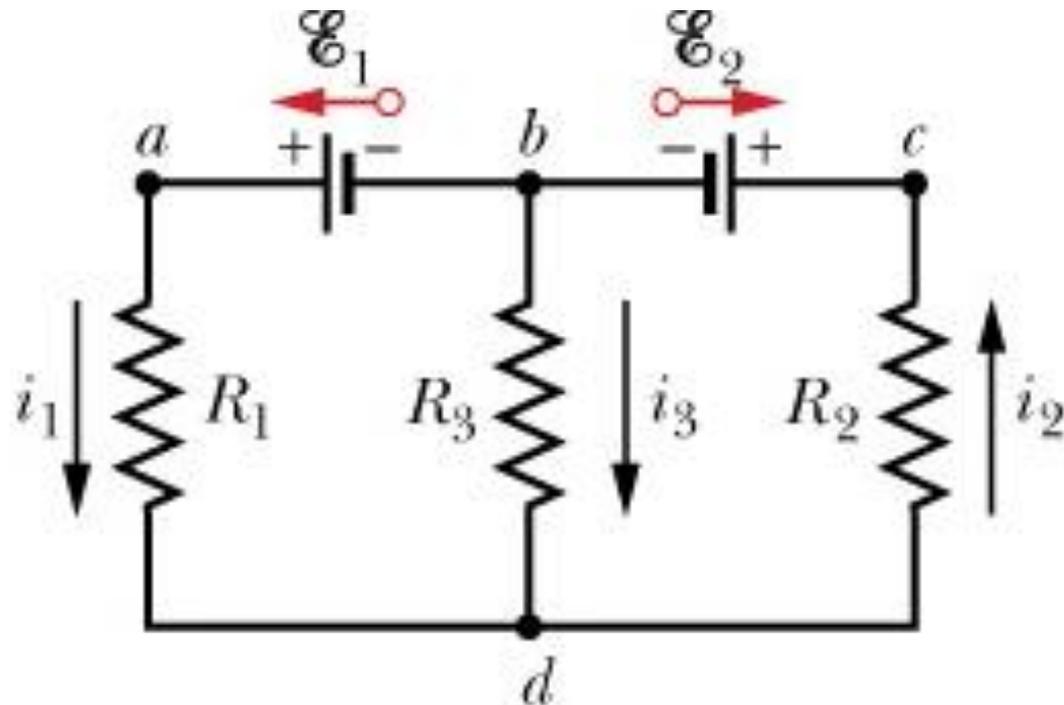**Note:** Equation (4) can be derived from the sum of (2) and (3), so we can use only two of the three equations above for such a multiloop circuit



### 3.7.3. Resistors in Series:

**Problem:** Calculate the resistance of resistors connected in series

We apply the Kirchhoff's rules in the clockwise direction:


- **Junction Rule:** When a potential difference  $V$  is applied across resistances connected in series, the resistances have identical currents  $i$ :

$$i = i_1 = i_2 = i_3$$


- **Loop Rule:** The sum of the potential differences across resistances is equal to the applied potential difference  $V$ :

$$\mathcal{E} - iR_1 - iR_2 - iR_3 = 0$$
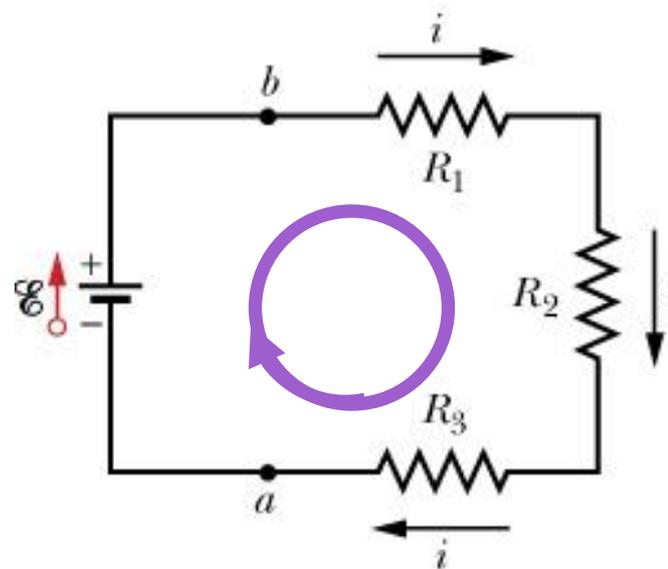
$$i = \frac{\mathcal{E}}{R_1 + R_2 + R_3}$$



(a)

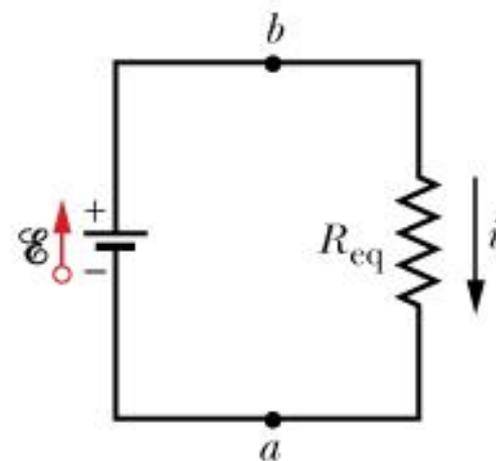

(b)


- If we replace three resistors by an equivalent resistor, so its resistance is:

$$\mathcal{E} - iR_{eq} = 0$$

$$R_{eq} = R_1 + R_2 + R_3$$

- For  $n$  resistors connected in series:

$$R_{eq} = \sum_{j=1}^n R_j$$

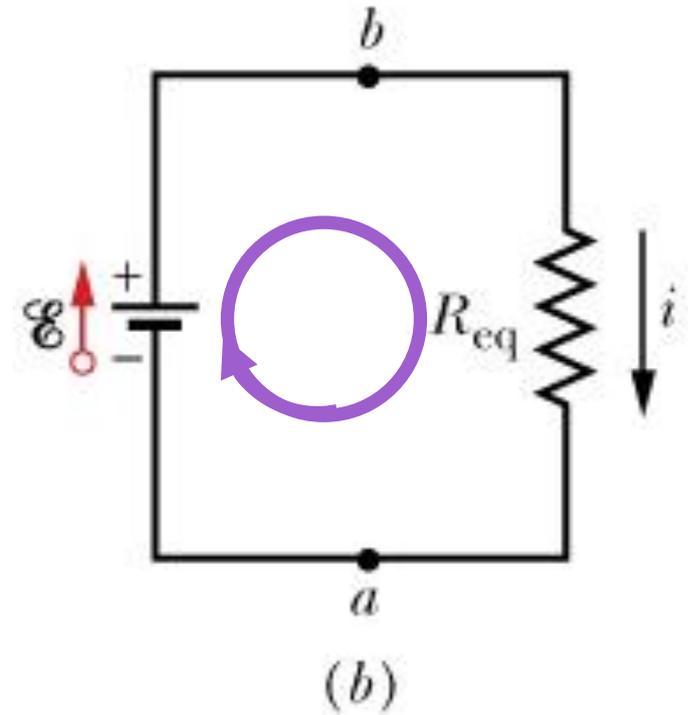

### 3.7.4. Resistors in Parallel:

**Problem:** Calculate the resistance of resistors connected in parallel

For resistors in parallel:



When a potential difference  $V$  is applied across resistances connected in parallel, the resistances all have that same potential difference  $V$ .

• **Junction Rule:**  $i = i_1 + i_2 + i_3$

$$i = V \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$

• **Loop Rule:** If we replace three resistors by an equivalent resistor:

$$\mathcal{E} - iR_{eq} = 0$$

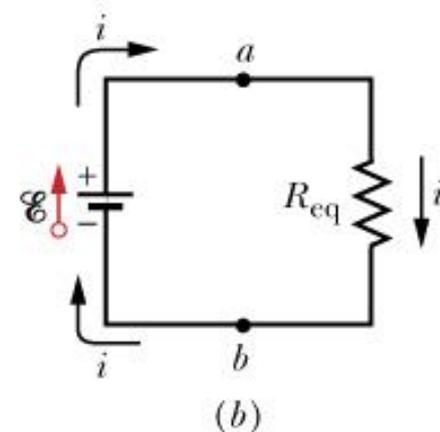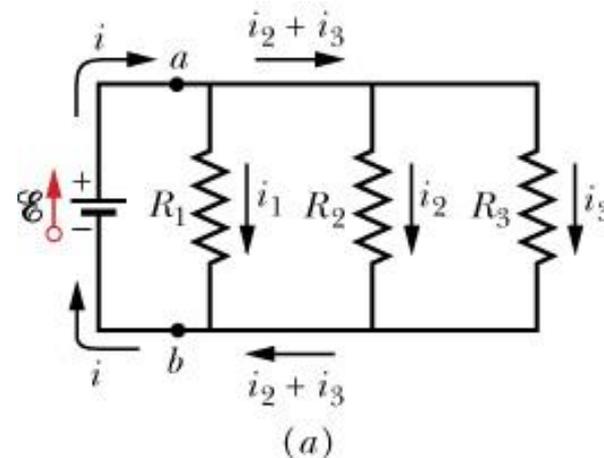

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

if  $n$  resistors in parallel:

$$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$$

# Series and Parallel Resistors and Capacitors

Series	Parallel	Series	Parallel
<u>Resistors</u>		<u>Capacitors</u>	
$R_{eq} = \sum_{j=1}^n R_j$	$\frac{1}{R_{eq}} = \sum_{j=1}^n \frac{1}{R_j}$	$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$	$C_{eq} = \sum_{j=1}^n C_j$
Same current through all resistors	Same potential difference across all resistors	Same charge on all capacitors	Same potential difference across all capacitors




**Sample Problem (p.718):** Electric fish are able to generate current with biological cells called *electroplaques*, which are physiological emf devices. The electroplaques in the type of electric fish known as a South American eel are arranged in **140 rows**, each row stretching horizontally along the body and each containing **5000** electroplaques. The arrangement is suggested in Figure a; each electroplaque has an emf  $\varepsilon$  of **0.15 V** and an internal resistance  $r$  of **0.25  $\Omega$** . The water surrounding the eel completes a circuit between the two ends of the electroplaque array, one end at the animal's head and the other near its tail.

(a) If the water surrounding the eel has resistance  $R_w = 800 \Omega$ , how much current can the eel produce in the water?


To solve this problem, we can simplify the circuit of Figure a by replacing combinations of emfs and internal resistances with equivalent emfs and resistances as shown in the following figures b, c, and d:

0.15 V

0.15 V

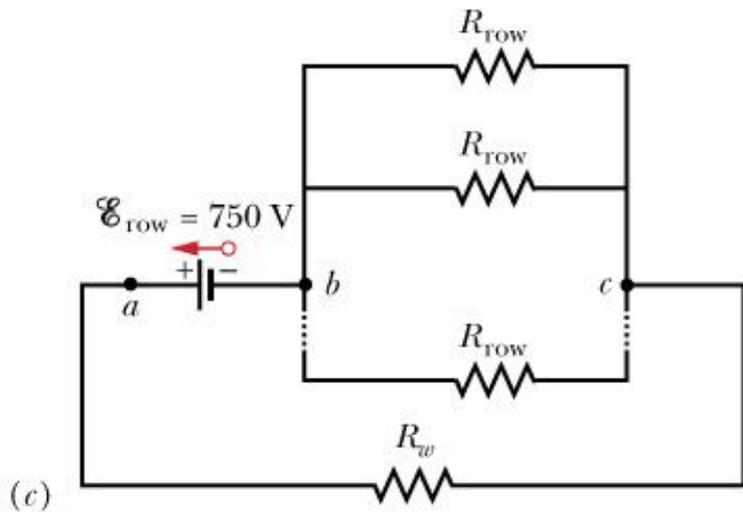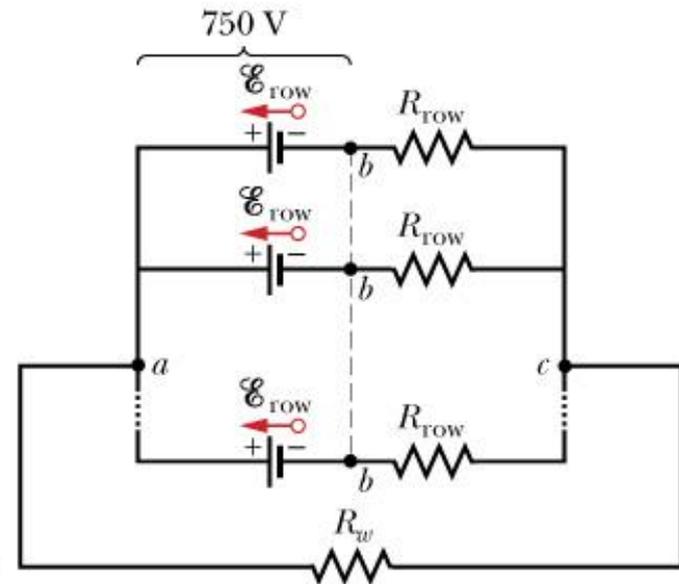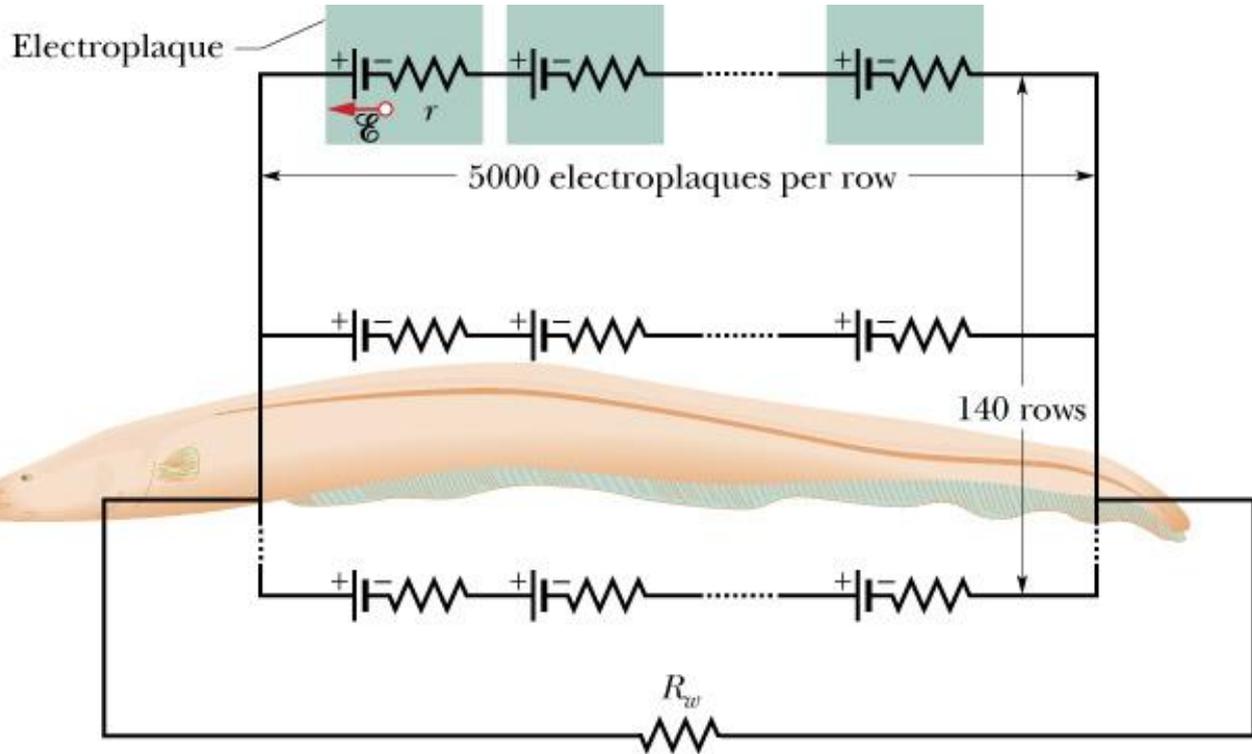
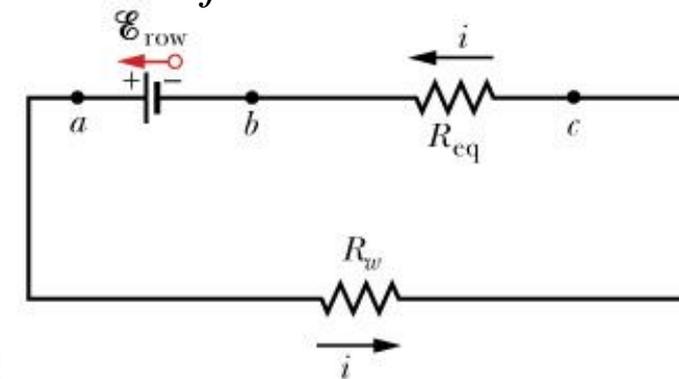
$$\frac{1}{R_{eq}} = \sum_{j=1}^{140} \frac{1}{R_j} = 140 \frac{1}{R_{row}}$$



(a)

(b)

(c)

(d)

The equivalent resistance:

$$R_{eq} = \frac{R_{row}}{140} = 8.93(\Omega)$$

Using the loop rule:


$$\varepsilon_{row} - iR_w - iR_{eq} = 0$$

$$i = \frac{\varepsilon_{row}}{R_w + R_{eq}} = \frac{750}{800 + 8.93} = 0.93(A)$$

Therefore, if the head or tail of the eel is near a fish, some of this current could pass along a narrow path through the fish, stunning or killing the fish

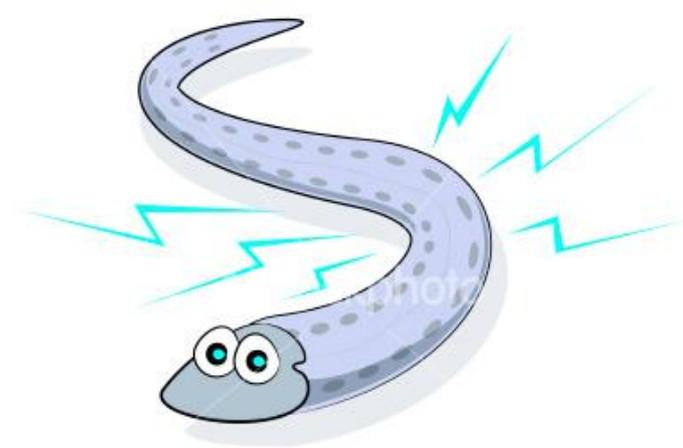(b) How much current  $i_{row}$  travels through each row of Figure a?

$$i_{row} = \frac{i}{140} = \frac{0.927}{140} = 6.6 \times 10^{-3} (A)$$




### 3.7.5. Calculating Potential Difference Between Two Points:

Usually we need to calculate potential difference between two points in a circuit. This section will show you how to do this in some common cases and other issues related to potential difference

• Calculate  $V_b - V_a$  in the figure:

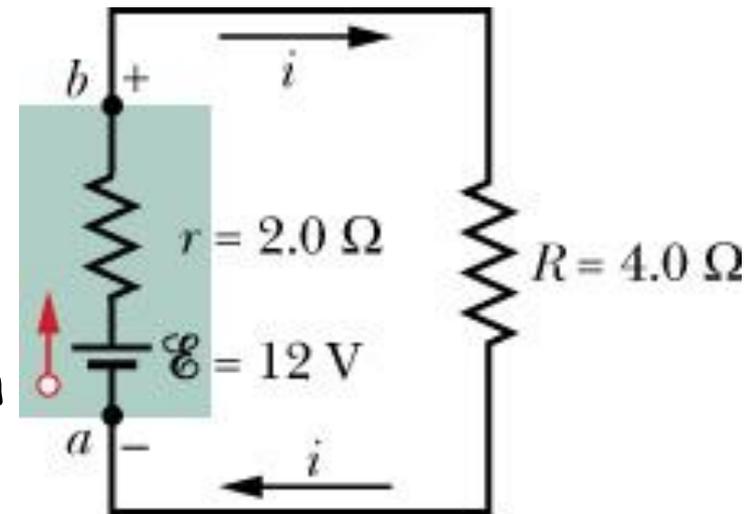We start at point a with potential  $V_a$ , when we pass through the battery's emf, the potential increases by  $\mathcal{E}$ , when we pass through the battery's internal resistance  $r$  the potential decreases by  $ir$ . We are then at point b with potential  $V_b$ :



$$V_a + \mathcal{E} - ir = V_b$$

So:

$$V_b - V_a = \mathcal{E} - ir; \quad i = \frac{\mathcal{E}}{r + R}$$

$$V_b - V_a = \frac{\mathcal{E}}{r + R} R = \frac{12}{2 + 4} 4 = 8(V)$$

$V_b - V_a$  is the terminal-to-terminal potential difference  $V$ :

$$V_b - V_a = \mathcal{E} - ir$$


So, for a real battery  $V$  is less  $\mathcal{E}$

For an ideal battery:  $V = \mathcal{E}$


**Grounding a circuit:** The figures show point a or b directly connected to ground (symbol: ). In this case, the potential is defined to be zero at the grounding point in the circuit

So, we have:

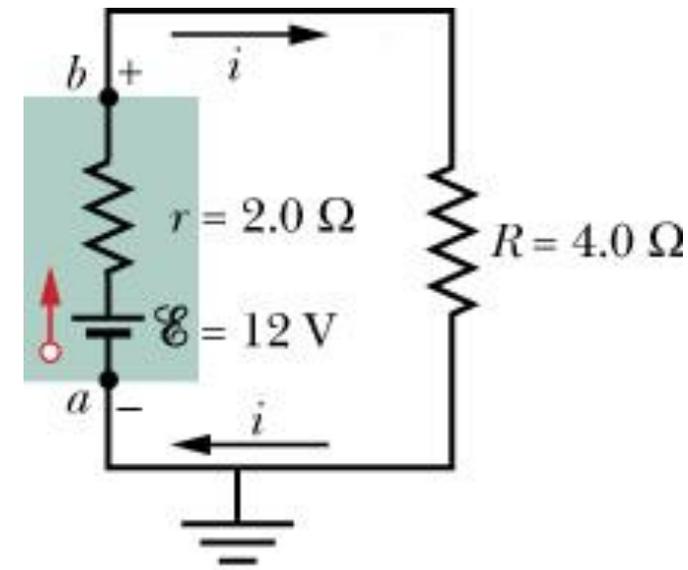- In Figure a,  $V_b - V_a = 8 \text{ V}$ ,  $V_a = 0 \rightarrow V_b = 8 \text{ V}$
- In Figure b,  $V_b = 0 \rightarrow V_a = -8 \text{ V}$



(a)

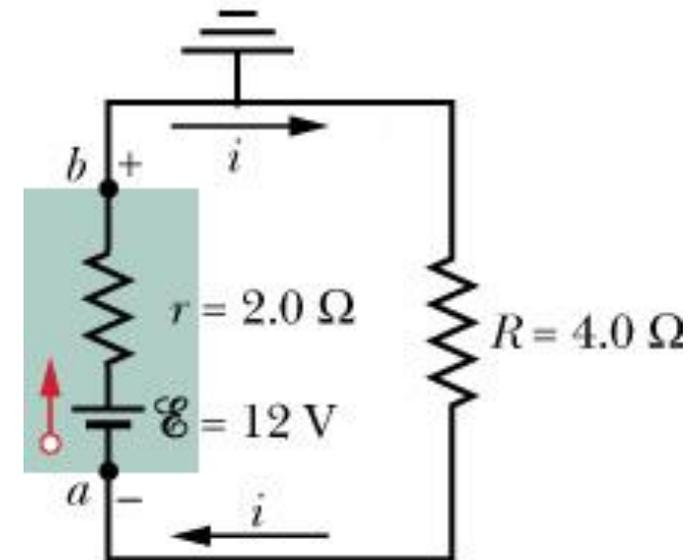

(b)

## The relationship between Power and Potential:

We will calculate work done by an emf device (e.g., a battery) on the charges to establish a current  $i$ ; the dissipation rate of energy due to the internal resistance  $r$  of the emf device and the power of the emf device

• The net rate  $P$  of energy transfer from the emf device to the charge carriers:

$$P = iV$$

• We also have:

$$V = \mathcal{E} - ir$$

$$P = i(\mathcal{E} - ir) = i\mathcal{E} - i^2r$$

• The term  $i^2r$  is the rate of energy transfer to thermal energy within the emf device:


$$P_r = i^2r$$

• The rate of energy transfer from the emf device both to the charges and to the thermal energy:

$$P_{emf} = i\mathcal{E}$$
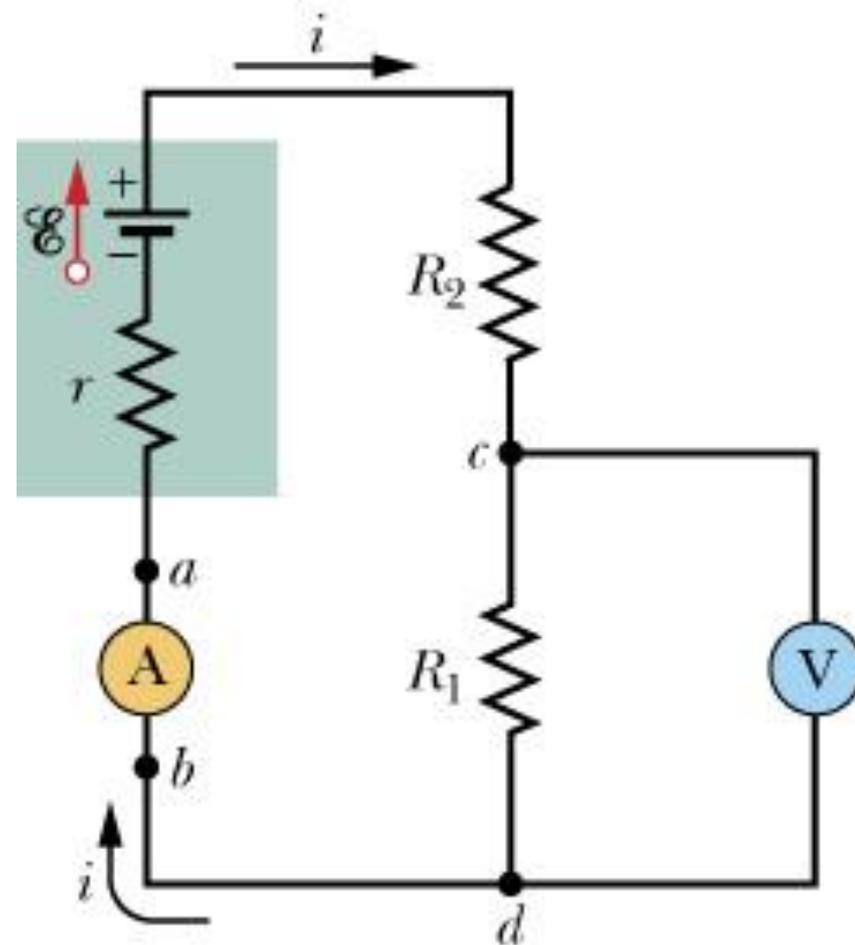
### 3.7.6. The Ammeter and the Voltmeter:

- An instrument that is used to measure currents is called **an ammeter**
- A meter to measure potential difference is called **a voltmeter**
- The figure shows how to set up an ammeter and a voltmeter in a circuit
- A meter can measure currents (ammeter), potential difference (voltmeter) and resistance (**ohmmeter**), by means of a switch, is called **a multimeter**



### 3.8. RC Circuits:

In this section we begin to study time-varying currents

#### 3.8.1. Charging a Capacitor:

- **An RC series circuit:** a circuit consists a capacitor  $C$ , an ideal battery and a resistor  $R$

- When  $S$  is closed on **a**,  $C$  is charged: the charge begins to flow between the capacitor plates and the battery terminals, establishing a current  $i$ .

When  $V_C = V_{\text{battery}} = \varepsilon$ , the current is zero


- Now, we examine the charging process:

- charge  $q(t)$ , potential difference  $V_C(t)$ , and current  $i(t)$ .

Using the loop rule:

$$\varepsilon - iR - V_C = 0 \Rightarrow \varepsilon - iR - \frac{q}{C} = 0$$
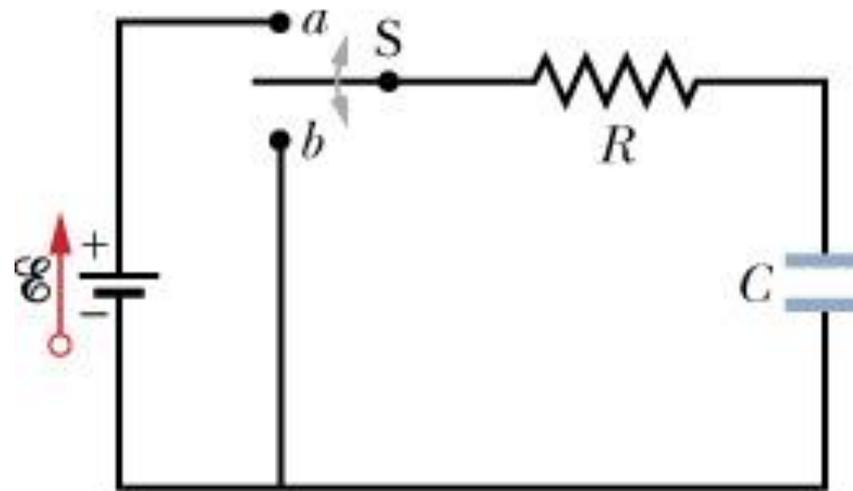
$$i = \frac{dq}{dt} \Rightarrow R \frac{dq}{dt} + \frac{q}{C} = \varepsilon \text{ (charging equation)}$$



The solution for the differential equation above is:

$$q = C\varepsilon(1 - e^{-t/RC})$$

(see text for solving the equation)


So, the current  $i(t)$ :

$$i = \frac{dq}{dt} = \left(\frac{\varepsilon}{R}\right)e^{-t/RC}$$


And the potential difference  $V(t)$  across the capacitor:

$$V_C = \frac{q}{C} = \varepsilon(1 - e^{-t/RC})$$

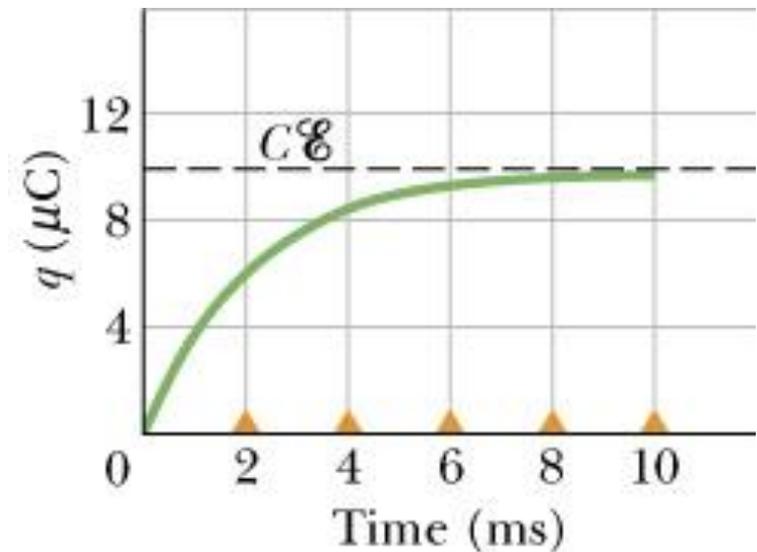**Note:** When the capacitor becomes fully charged as  $t \rightarrow \infty$ :  $q = C\varepsilon$ ,  $i = 0$ , and  $V_C = \varepsilon$



(a)

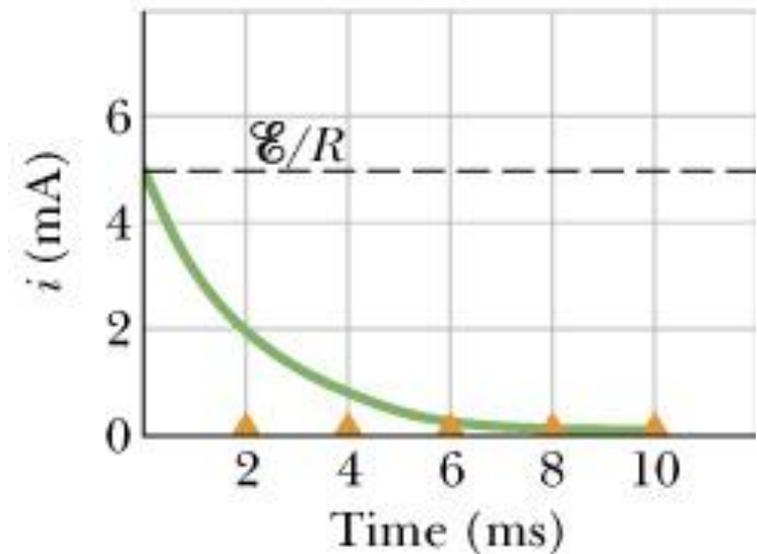

(b)

The time constant:

$$\tau = RC \quad (\text{Unit: s})$$

At  $t = \tau = RC$ :

$$q = C\varepsilon(1 - e^{-1}) = 0.63C\varepsilon$$

During the first time  $\tau$ , the charge increases from zero to **63%** of its final value  $C\varepsilon$

The greater  $\tau$  is the greater the charging time

### 3.8.2. Discharging a Capacitor:

After being fully charged, the capacitor has a potential  $V_0 = \varepsilon$ , we switch  $S$  from  $a$  to  $b$ , so the capacitor discharges through resistor  $R$ . Using the loop rule:

$$R \frac{dq}{dt} + \frac{q}{C} = 0 \quad (\text{discharging equation})$$

The solution for this equation is:

$$q = q_0 e^{-t/RC}$$

Where:

$$q_0 = CV_0$$

At  $t = \tau = RC$ , the charge is reduced to  $q_0 e^{-1}$  or about 37% of the initial value

The current  $i(t)$ :

$$i = \frac{dq}{dt} = -\left(\frac{q_0}{RC}\right)e^{-t/RC}$$

The potential difference  $V_C(t)$ :

$$V_C = V_0 e^{-t/RC}$$





**Homework:** 2, 5, 7, 10, 17, 22, 24, 30, 34, 44, 45, 54,  
57, 60, 65 (pages 726-731)